ADI (Analog Devices, Inc.)

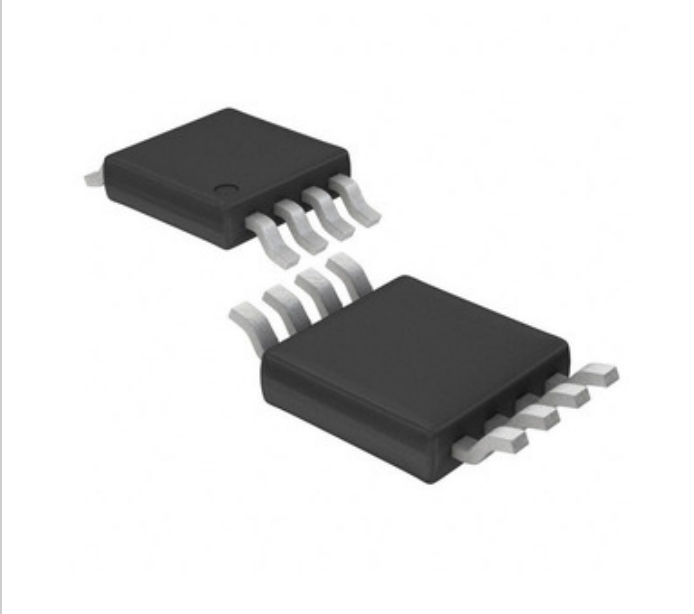

□□□□□□□□□□□□ □□□□□□□□ □□□□ □□□□□□□□□□□□□□□□. □□□□□□□ □□□□□□□□ □□□□□□□□□□ □□□□□□□□□.

LTC4359CMS8#PBF

□□□□□□ □□□□□□:	LTC4359CMS8#PBF
□□□□□□□□□□□ / □□□□□□:	ADI (Analog Devices, Inc.)
□■■■■■■■ ■■■■■■	IC OR CTRLR N+1 8MSOP
□□□□□□□□□ □□□□□□:	1.LTC4359CMS8#PBF.pdf 2.LTC4359CMS8#PBF.pdf 3.LTC4359CMS8#PBF.pdf 4.LTC4359CMS8#PBF.pdf
RoHs □□□□□□□	□□□□□□□ □□□□□ / RoHS Compliant
□□□□□□□ □□□□□□□□□□□	22497 pcs stock
□□□□□□□	□□□□ □□□□□
□□□□□□□□□□ □□□	DHL/Fedex/TNT/UPS/EMS

□□□□□□□□ □□□□□□□□

□□□□□□□□□□□□□□□ LTC4359CMS8#PBF

□□□□□□ □□□□□□	LTC4359CMS8#PBF
□□□□□□□□□□□	ADI (Analog Devices, Inc.)
□□□□□□	IC OR CTRLR N+1 8MSOP
□□□□□□□ □□□□□□□□□□ □□□□□□□ / ROHS □□□□□□□	□□□□□□□ □□□□□ / RoHS Compliant
□□□□□□□□□ □□□□□□□□□□□□□□	22497 pcs
□□□□□□□□□ □□□□□□□	1.LTC4359CMS8#PBF.pdf 2.LTC4359CMS8#PBF.pdf 3.LTC4359CMS8#PBF.pdf 4.LTC4359CMS8#PBF.pdf
□□□□□ - □□□□□□□□□	4 V ~ 80 V
□□□□	N+1 ORing Controller
□□□□□□□□□□□ □□□□□□□□□□□ □□□□□□	8-MSOP
□□□□□	-
□□□□□□□□□□□ - □□□□□□□: □□□□□□□□□	N:1
□□□□□□□	Tube
□□□□□□ / □□□□□	8-TSSOP, 8-MSOP (0.118", 3.00mm Width)
□□□□□□□□□□ □□□□□□□□□□□	0°C ~ 70°C (TA)
□□□□□□□□□ □□□□	Surface Mount
□□□□□□□□□□ □□□□□□□□□□□□□□ □□□□ (MSL)	1 (Unlimited)
□□□□□□□ □□□□□□□□□□ □□□□□□□□ / ROHS □□□□□□□	Lead free / RoHS Compliant
□□□□ □□□□□□ (□□)	No
FET □□□□	N-Channel
□□□□□□□□ □□□□□□□	OR Controller N+1 ORing Controller N-Channel N:1 8-MSOP
□□□□□□□□□ □□□ - □□□□□□□□□	200µs
□□□□□□□□□□ □□□ - OFF	300ns
□□□□□□□□□ - □□□□□□□□□	150µA
□□□□□□□□□ - □□□□□□□□□□ (□□□□□□□□□□□)	220µA
□□□□ □□□□□□ □□□□□□	LTC4359
□□□□□□□□□□	Automotive, Redundant Power Supplies, Telecom Infrastructure

□□□□□□□□□□□□□□

Tags

ADI (Analog Devices, Inc.) LTC4359CMS8#PBF	LTC4359CMS8#PBF □□□□□□□□□□□□	LTC4359CMS8#PBF □□□□□□□□□□□
LTC4359CMS8#PBF □□□□	LTC4359CMS8#PBF □□□□□□□□	LTC4359CMS8#PBF □□□□□□□□□□□□
LTC4359CMS8#PBF PDF Datasheet	LTC4359CMS8#PBF Download Datasheet	LTC4359CMS8#PBF Datasheet
LTC4359CMS8#PBF □□□□□□□	□□□□□□□□ LTC4359CMS8#PBF	□□□□□□□□ ADI (Analog Devices, Inc.) LTC4359CMS8#PBF
ADI (Analog Devices, Inc.) LTC4359CMS8#PBF	ADI (Analog Devices, Inc.) □□□□□□□□□□□	ADI (Analog Devices, Inc.) □□□□□□□□□□□□
ADI (Analog Devices, Inc.) LTC4359CMS8#PBF	AD LTC4359CMS8#PBF	ADI (Analog Devices, Inc.) LTC4359CMS8#PBF
Analog Devices Inc. LTC4359CMS8#PBF	Analog Devices, Inc. LTC4359CMS8#PBF	

□□□□□□□ □□□□□□□□□□

LTC4359HMS8#TRPBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 8MSOP
□■■■■■■■: 14415 pcs
RFQ

LTC4359HDCB#TRPBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 6DFN
□■■■■■■■: 29029 pcs
RFQ

LTC4358IFE#TRPBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 16TSSOP
□■■■■■■■: 28428 pcs
RFQ

LTC4358IFE#PBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 16TSSOP
□■■■■■■■: 16199 pcs
RFQ

LTC4359CDCB#TRMPBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 6DFN
□■■■■■■■: 31367 pcs
RFQ

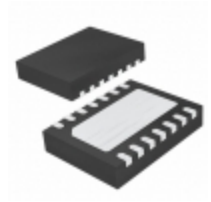

LTC4358IDE#TRPBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 14DFN
□■■■■■■■: 27182 pcs
RFQ

LTC4359HS8#PBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IDEAL DIODE CONTROLLER WITH REVE
□■■■■■■■: 17562 pcs
RFQ

LTC4359CMS8#TRPBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 8MSOP
□■■■■■■■: 17693 pcs
RFQ

LTC4359HDCB#TRMPBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 6DFN
□■■■■■■■: 29788 pcs
RFQ

LTC4358IFE
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC POWER MANAGEMENT
□■■■■■■■: 4193 pcs
RFQ

LTC4359CDCB#TRPBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 6DFN
□■■■■■■■: 39228 pcs
RFQ

LTC4359HMS8#PBF
□□□□□□□□□□□□: ADI (Analog Devices, Inc.)
□□□□□□: IC OR CTRLR N+1 8MSOP
□■■■■■■■: 14137 pcs
RFQ

□□□□□□□□ □□□□□□□□ © 2020 □□□□□□□□□□□ □□□□□□□□□□□□□ □□□□□ □□□□□□□□□□□□

□□.□□□□□: Info@infinity-electronic.com